







**LAB 05*****Using multiple timers to develop the logic for Traffic signal*****OBJECTIVE:**

- To practice the use of multiple Timer instructions and sequences
- To develop the ladder logic
- To simulate the logic
- To download the program in PLC and check the results in real time


**TASK:**

- In this application the PLC is used to control the 4-way traffic signals.
- Traffic signal starts working after pressing the push button.
- The sequence of the lights are  
RED → YELLOW → GREEN → YELLOW → RED.
- Red light will be on for 5 seconds.
- Then after that yellow light will be on for 3 seconds
- Green light for 5seconds.
- After than yellow light will be on & then red & this whole process will be repeated.


# SIMATIC MANAGER STEP 7 PROGRAM:

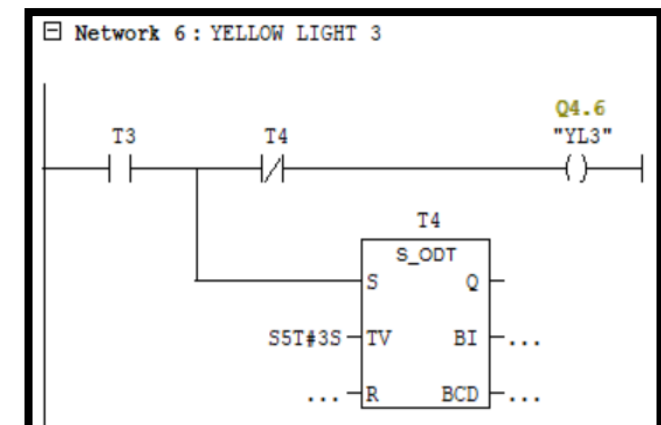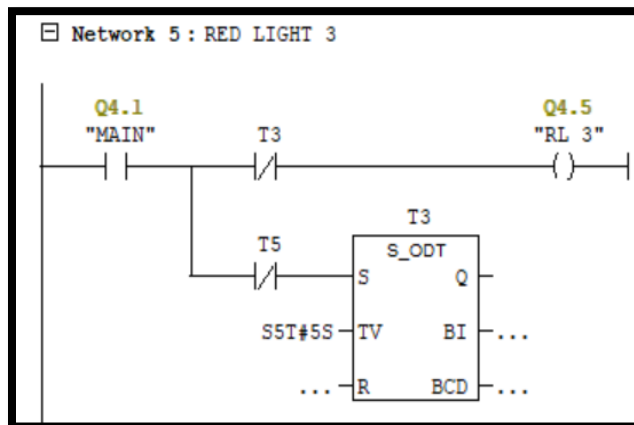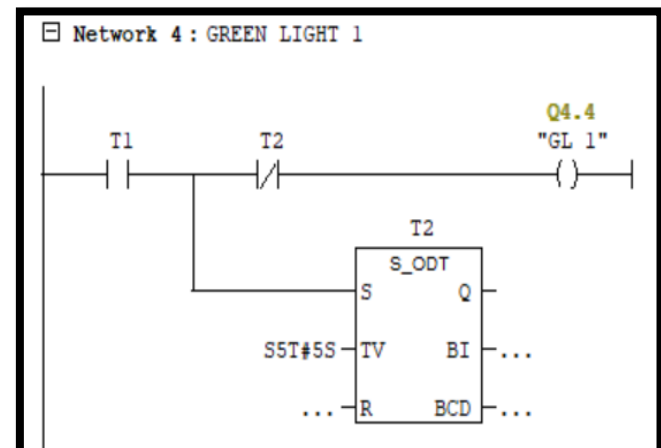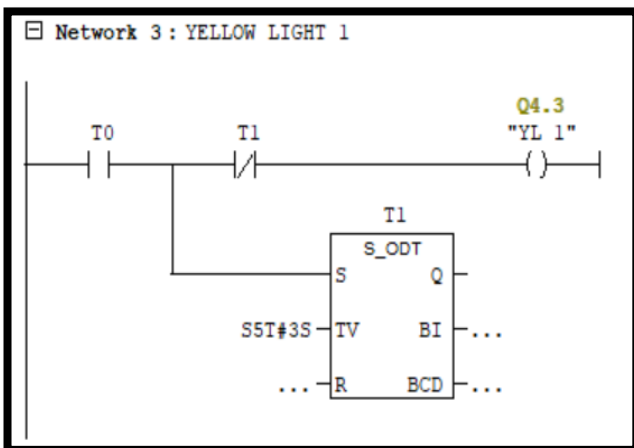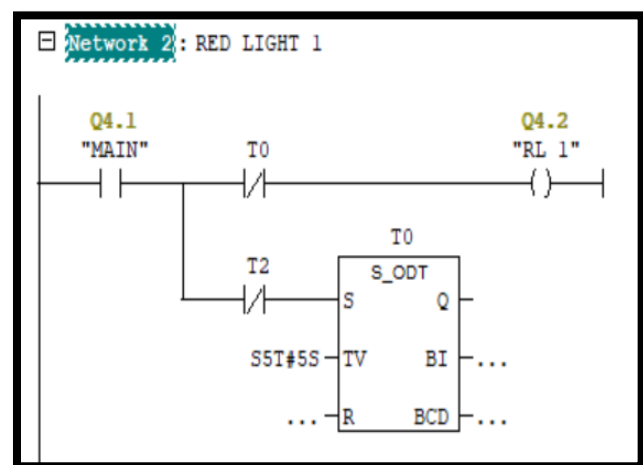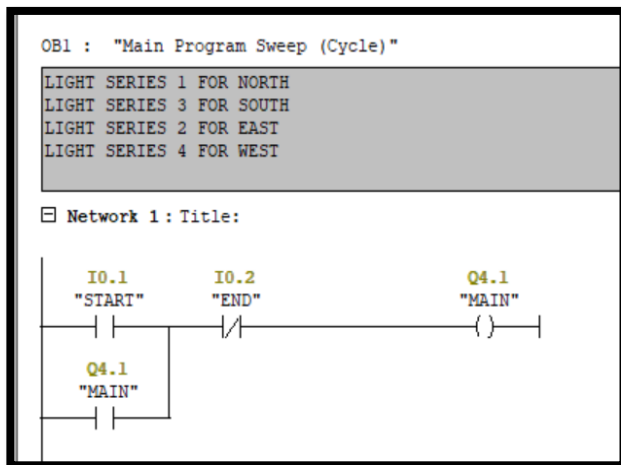


Network 7 : GREEN LIGHT 3

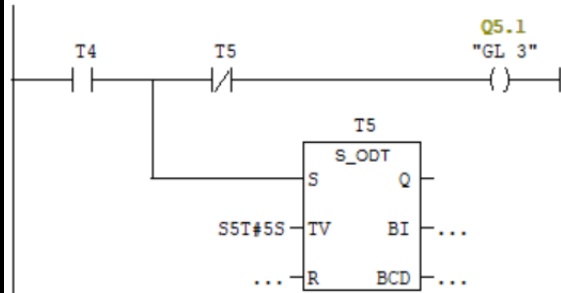


Network 8 : GREEN LIGHT 2

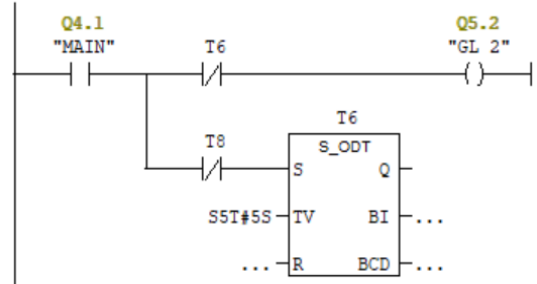


Network 9 : YELLOW LIGHT 2

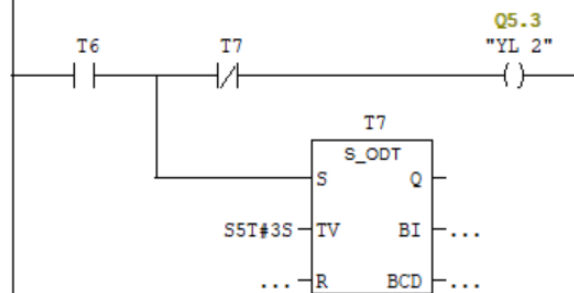


Network 10 : RED LIGHT 2

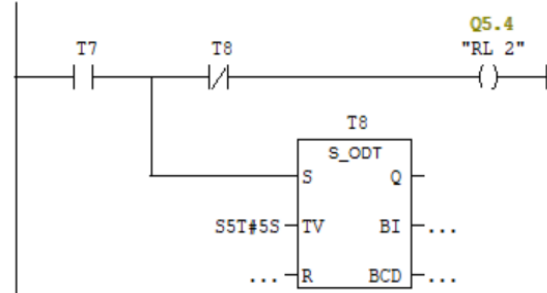


Network 11 : GREEN LIGHT 4

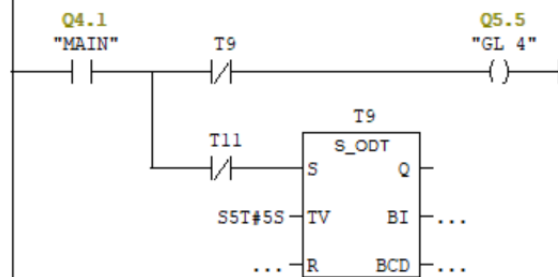



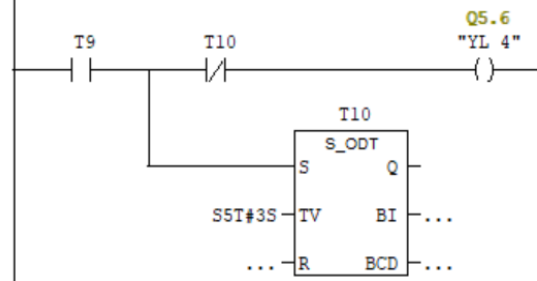



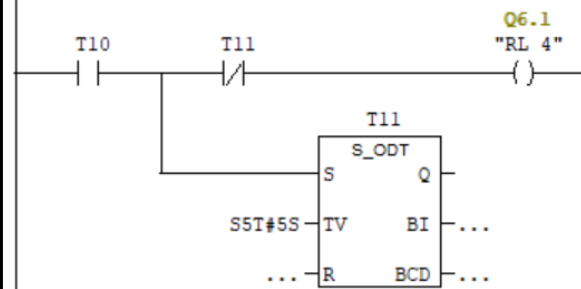







Network 12 : YELLOW LIGHT 4



Network 13 : RED LIGHT 4



## VARIABLE TABLE

		Address	Symbol	Display format	Status value
1		Q 4.1	"MAIN"	BOOL	 true
2		Q 4.2	"RL 1"	BOOL	 false
3		Q 4.3	"YL 1"	BOOL	 false
4		Q 4.4	"GL 1"	BOOL	 true
5		Q 4.5	"RL 3"	BOOL	 false
6		Q 4.6	"YL3"	BOOL	 false
7		Q 5.1	"GL 3"	BOOL	 true
8		Q 5.2	"GL 2"	BOOL	 false
9		Q 5.3	"YL 2"	BOOL	 false
10		Q 5.4	"RL 2"	BOOL	 true
11		Q 5.5	"GL 4"	BOOL	 false
12		Q 5.6	"YL 4"	BOOL	 false
13		Q 6.1	"RL 4"	BOOL	 true